

## ECAT Physics Chapter 12 Electrostatics Online Test

Sr	Questions	Answers Choice
1	Thermocouple is an arrangement of two different metals	<p>A. To convert heat energy in to electrical energy</p> <p>B. To produce more heat</p> <p>C. To convert heat energy into chemical energy</p> <p>D. To convert electric energy in to heat energy</p>
2	Current provided by a battery is maximum when	<p>A. Internal resistance equal to external resistance</p> <p>B. Internal resistance is greater than external resistance</p> <p>C. Internal resistance is less then external resistance</p> <p>D. None of these</p>
3	The thermistors are usually made of	<p>A. Metals with low temperature coefficient of resistivity</p> <p>B. Metals with high temperature coefficient of resistivity</p> <p>C. Metal oxides with high temperature coefficient of resistivity</p> <p>D. Semi conducting materials having low temperature coefficient of resistivity</p>
4	In Pakistan electricity is supplied for domestic use at 220 V, it is supplied at 110 V in USA. If the resistance of a 60 W bulb for use in Pakistan is R, the resistance of a 60 W bulb for use in USA will be	<p>A. 2 R</p> <p>B. <math>R/4</math></p> <p>C. <math>R/2</math></p> <p>D. R</p>
5	When three identical bulbs of 60 watt, 200 volt rating are connected in series to a 200 volt supply, the power drawn by them will be	<p>A. 180 watt</p> <p>B. 10 watt</p> <p>C. 20 watt</p> <p>D. 60 watt</p>
6	Which of the following does not obey ohm's law?	<p>A. Copper</p> <p>B. Al</p> <p>C. Diode</p> <p>D. None</p>
7	Battery is charged in motor cars, which is based on	<p>A. Chemical effect</p> <p>B. Magnetic effect</p> <p>C. Electric effect</p> <p>D. None</p>
8	The minimum resistance that can be obtained by connecting 5 resistance of $\frac{1}{4}\Omega$ each is	<p>A. <math>\frac{4}{5}\Omega</math></p> <p>B. <math>\frac{5}{4}\Omega</math></p> <p>C. <math>20\Omega</math></p> <p>D. <math>0.05\Omega</math></p>
9	The resistance of an incandescent lamp is	<p>A. Smaller when switched on</p> <p>B. Greater when switched off</p> <p>C. The same whether it is switch off or switch on</p>

D. Greater when switched on

10	A current of 1.6 A is passed through a solution of $\text{CuSO}_4$ . How many $\text{Cu}^{2+}$ ions are liberated in one minute?	A. $3 \times 10^{20}$ B. $3 \times 10^{10}$ C. $6 \times 10^{20}$ D. $6 \times 10^{10}$
11	A heater coil rated at (1000 W - 200 V) is connected to 110 volt line. What will be the power consumed?	A. 200 W B. 302.5 C. 250 W D. 350 W
12	The colour sequence in a carbon resistor is red, brown, orange and silver. The resistance of the resistor is	A. $21 \times 10^3 \Omega$ B. $23 \times 10^1 \Omega$ C. $21 \times 10^3 \Omega$ D. $12 \times 10^3 \Omega$
13	For two resistance wires joined in parallel, the resultant resistance is $\frac{6}{5}$ ohm. When one of the resistance wire breaks, the effective resistance becomes 2 ohm. The resistance of the broken wire is	A. $\frac{3}{5}$ ohm B. 2 ohm C. $\frac{6}{5}$ ohm D. 3 ohm
14	A uniform resistance wire of Length L and diameter d has a resistance R. Another wire of same material has length, 4L and diameter 2d, the resistance will be	A. 2 R B. R C. $\frac{R}{2}$ D. $\frac{R}{4}$
15	Calculate the amount of charge flowing in 2 minutes in a wire of resistance $10 \Omega$ when a potential difference of 20 V is applied between its ends	A. 120 C B. 240 C C. 20 C D. 4 C