

## ECAT Physics Online Test

Sr	Questions	Answers Choice
1	In gases, the charge carriers are:	A. Electrons B. Positive ions C. Negative ions D. Both A and C <b>E. Both A and B</b>
2	Thermocouple is an arrangement of two different metals	<b>A. To convert heat energy in to electrical energy</b> B. To produce more heat C. To convert heat energy into chemical energy D. To convert electric energy in to heat energy
3	Current provided by a battery is maximum when	<b>A. Internal resistance equal to external resistance</b> B. Internal resistance is greater than external resistance C. Internal resistance is less then external resistance D. None of these
4	The thermistors are usually made of	A. Metals with low temperature coefficient of resistivity B. Metals with high temperature coefficient of resistivity <b>C. Metal oxides with high temperature coefficient of resistivity</b> D. Semi conducting materials having low temperature coefficient of resistivity
5	In Pakistan electricity is supplied for domestic use at 220 V, it is supplied at 110 V in USA. If the resistance of a 60 W bulb for use in Pakistan is R, the resistance of a 60 W bulb for use in USA will be	A. 2 R <b>B. R/4</b> C. R/2 D. R
6	When three identical bulbs of 60 watt, 200 volt rating are connected in series to a 200 volt supply, the power drawn by them will be	<b>A. 180 watt</b> B. 10 watt C. 20 watt D. 60 watt
7	Which of the following does not obey ohm's law?	A. Copper B. Al C. Diode <b>D. None</b>
8	Battery is charged in motor cars, which is based on	<b>A. Chemical effect</b> B. Magnetic effect C. Electric effect D. None
9	The minimum resistance that can be obtained by connecting 5 resistance of $\frac{1}{4}\Omega$ each is	A. $\frac{4}{5}$ B. $\frac{5}{4}$ C. 20 <b>D. 0.05</b>

		</span>
10	The resistance of an incandescent lamp is	A. Smaller when switched on B. Greater when switched off C. The same whether it is switch off or switch on D. Greater when switched on
11	A current of 1.6 A is passed through a solution of $\text{CuSO}_4$ . How many $\text{Cu}^{2+}$ ions are liberated in one minute?	A. $3 \times 10^{20}$ B. $3 \times 10^{10}$ C. $6 \times 10^{20}$ D. $6 \times 10^{10}$
12	A heater coil rated at (1000 W - 200 V) is connected to 110 volt line. What will be the power consumed?	A. 200 W B. 302.5 C. 250 W D. 350 W
13	The colour sequence in a carbon resistor in red, brown, orange and silver. The resistance of the resistor is	A. $21 \times 10^3 \Omega \pm 10\%$ B. $23 \times 10^1 \Omega \pm 10\%$ C. $21 \times 10^3 \Omega \pm 5\%$ D. $12 \times 10^3 \Omega \pm 5\%$
14	For two resistance wires joined in parallel, the resultant resistance is $\frac{6}{5}$ ohm. When one of the resistance wire breaks, the effective resistance becomes 2 ohm. The resistance of the broken wire is	A. $\frac{3}{5}$ ohm B. 2 ohm C. $\frac{6}{5}$ ohm D. 3 ohm
15	A uniform resistance wire of Length L and diameter d has a resistance R. Another wire of same material has length, 4L and diameter 2d, the resistance will be	A. 2 R B. R C. $\frac{R}{2}$ D. $\frac{R}{4}$
16	Calculate the amount of charge flowing in 2 minutes in a wire of resistance $10 \Omega$ when a potential difference of 20 V is applied between its ends	A. 120 C B. 240 C C. 20 C D. 4 C
17	$10^6$ electrons are moving through a wire per second, the current developed is	A. $1.6 \times 10^{-19}$ B. 1 A C. $1.6 \times 10^{-15}$ A D. $10^{-6}$ A
18	The resistance of 20 cm long wire is $10 \Omega$ . When the length is changed to 40 cm. The new resistance is	A. $10 \Omega$ B. $20 \Omega$ C. $30 \Omega$ D. $40 \Omega$
19	If two bulbs one of 60 W and other of 100 W are connected in parallel, then which one of the following will flow more?	A. 60 W bulb B. 100 W bulb C. Both equally D. None of these
20	Which one of the following causes production of heat when current is set up in a wire?	A. Fall of electrons from higher orbits to lower orbits B. Inter-atomic collisions C. Inter-electron collisions D. Collisions of conduction electron with atoms
		A. $3R$ B. $3R$ C. $3R$ D. $3R$

21	Three resistors of resistance R each are combined in various ways. Which of the following cannot be obtained?	<p>A. <math>R</math></p> <p>B. <math>2R/4</math></p> <p>C. <math>R/3</math></p> <p>D. <math>2R/3</math></p>
22	The resistance of the given conductor can be increased by	<p>A. Increasing the area</p> <p>B. Changing resistivity</p> <p>C. Decreasing the length</p> <p>D. None of the above because change does not matter because in any case the volume remains the same</p>
23	A 100 W, 200 V bulb is connected to a 160 volts supply. The actual power consumption would be	<p>A. 64 W</p> <p>B. 80 W</p> <p>C. 100 W</p> <p>D. 125 W</p>
24	A 60 W bulb operates on 220 V supply. The current flowing through the bulb is	<p>A. <math>11/3</math> A</p> <p>B. 3 A</p> <p>C. <math>3/11</math> A</p> <p>D. 6</p>
25	At ordinary temperature, an increase in temperature increases the conductivity of	<p>A. Conductor</p> <p>B. Semiconductor</p> <p>C. Insulator</p> <p>D. Alloy</p>
26	Potentiometer is more sensitive than voltmeter, because	<p>A. Voltmeter has a very high resistance</p> <p>B. Voltmeter has a very low resistance</p> <p>C. Potentiometer does not draw any current from a source of unknown potential difference</p> <p>D. Potentiometer is sensitive</p>
27	A car battery has e.m.f 12 volt and internal resistance $5 \times 10^{-2}$ ohm. If it draws 60 ampere current, the terminal voltage of the battery will be	<p>A. 5 volt</p> <p>B. 3 volt</p> <p>C. 15 volt</p> <p>D. 9 volt</p>
28	Specific resistance of a wire depends upon	<p>A. Length</p> <p>B. Cross-section area</p> <p>C. Mass</p> <p>D. None</p>
29	Cause of heat production in a current carrying conductor is	<p>A. Collisions of free electrons with one another</p> <p>B. High drift speed of free electrons</p> <p>C. Collisions of free electrons with atoms or ions of conductor</p> <p>D. High resistance value</p>
30	In a building, there are 15 bulbs of 40 watts, 5 bulbs of 100 watts, 5 fans of 80 watts and a heater of 1 kilowatt. The voltage of the electric main is 220 volts. The minimum efficiency of the main fuse of the building will be	<p>A. 0.4 A</p> <p>B. 11.4 A</p> <p>C. 9.8 A</p> <p>D. 10.6 A</p>