

## ECAT Pre General Science Physics Chapter 16 Alternating Current Online Test

Sr	Questions	Answers Choice
1	The closed loop gain of the non-inverting amplifier is given by	A. $G = \frac{R_2}{R_1}$ B. $G = -\frac{R_2}{R_1}$ C. $G = 1 + \frac{R_2}{R_1}$ D. $G = 1 + \frac{R_1}{R_2}$
2	The closed loop gain of the inverting amplifier is written as	A. $G = \frac{R_2}{R_1}$ B. $G = 1 + \frac{R_2}{R_1}$ C. $G = -\frac{R_2}{R_1}$ D. $G = 1 - \frac{R_2}{R_1}$
3	The open loop gain of OP-AMP is of the order of	A. $10^2$ B. $10^3$ C. $10^4$ D. $10^5$
4	The value of output resistance of OP-AMP is of the order of	A. few ohms B. few hundred ohms C. several kilo ohms D. several mega ohms
5	Due to the high value of the input resistance, practically, the value of the current which flows between the input terminals is	A. zero B. small C. large D. very large
6	The value of the input resistance of OP-AMP is of the order of	A. few ohms B. few hundred ohms C. several kilo ohms D. several mega ohms
7	The input resistance of the OP-AMP is the resistance between the	A. (-) input and output B. (+) input and output C. (-) and (+) inputs D. between any inputs
8	A signal is amplified at the output without any change of phase, if it is applied at the	A. inverting input B. non-inverting input C. at any of the input D. none of these
9	A signal appears after amplification, at the output terminal with a phase shift of $180^\circ$ , if it is applied at	A. inverting input B. non-inverting input C. any one of the input terminal D. none of them
10	OP-AMP has the following input terminals	A. one B. two C. three D. four
11	The amplifier which is used to perform mathematical operations electronically is known as	A. calculator B. OP-AMP C. computer D. any one of them
12	When a transistor is used as a switch the circuit in which the current is to be switched OFF and ON, is connected between the	A. base and emitter B. collector and emitter C. base and collector D. any one of these
13	The emitter-base junction of a transistor is forward-biased and collector-base junction is reverse-biased. If the base current is increased, its	A. $I_C$ will decrease B. $V_{CE}$ will increase C. $I_C$ will increase D. $V_{CC}$ will increase
14	When the emitter-base junction of a transistor is reverse biased, collector current	A. Reverses B. Increases C. — D. —

		<p>C. Decreases</p> <p>D. Stops</p>
15	The value of current gain of n-p-n transistor is of the order of	<p>A. tens</p> <p>B. hundreds</p> <p>C. thousands</p> <p>D. ten thousands</p>
16	For a n-p-n transistor, the conventional current equation can be written as	<p>A. <math>I_E = I_C + I_B</math></p> <p>B. <math>I_C = I_E + I_B</math></p> <p>C. <math>I_C = I_E - I_B</math></p> <p>D. <math>I_E = I_C - I_B</math></p>
17	In a normally biased n-p-n transistor, an electron current $I_E$ flows from the	<p>A. emitter into the base</p> <p>B. collector into the base</p> <p>C. base into collector</p> <p>D. none of these</p>
18	In n-p-n transistor, emitter base junction is kept	<p>A. reversed</p> <p>B. forward biased</p> <p>C. may be reversed or may be forward biased</p> <p>D. none of these</p>
19	For normal operation of transistor, the batteries	<p>A. <math>V_{CC}</math> is of much lower value than <math>V_{BB}</math></p> <p>B. <math>V_{CC}</math> is of much higher value than <math>V_{BB}</math></p> <p>C. <math>V_{CC}</math> is equal to <math>V_{BB}</math></p> <p>D. none of these</p>
20	For the normal operation of the transistor, its	<p>A. emitter-base and collector base junctions are forward biased</p> <p>B. emitter-base junction is reversed biased and collector base junction is forward biased</p> <p>C. emitter-base junction is forward biased and collector-base junction is reverse biased</p> <p>D. any one of these</p>
21	Which of the following has a great concentration of impurity	<p>A. base</p> <p>B. emitter</p> <p>C. collector</p> <p>D. none of these</p>
22	In a transistor, the central region is called	<p>A. collector</p> <p>B. emitter</p> <p>C. base</p> <p>D. none of them</p>
23	In a transistor, if the central region is n-type, then this type of transistor is known as	<p>A. n-p-n transistor</p> <p>B. p-n-p transistor</p> <p>C. either of these</p> <p>D. none of these</p>
24	In a transistor, if the central region is p-type then this type of transistor is known as	<p>A. p-n-p transistor</p> <p>B. n-p-n transistor</p> <p>C. either of these</p> <p>D. none of these</p>
25	Which of the following diodes can operate in the reverse biased condition	<p>A. photo diode</p> <p>B. light emitting diode</p> <p>C. photo voltaic cell</p> <p>D. none of these</p>
26	Which of the following diode is used to derive the current in external circuit when light is incident in the circuit	<p>A. photo diode</p> <p>B. light emitting diode</p> <p>C. photo voltaic cell</p> <p>D. none of these</p>
27	Which of the following diode is used for the detection of light	<p>A. photo diode</p> <p>B. light emitting diode</p> <p>C. photo voltaic cell</p> <p>D. all of them</p>
28	In which of the following diodes when an electron combines with a hole during the forward biasing, photon of visible light is emitted.	<p>A. photo diode</p> <p>B. light emitting diode</p> <p>C. photo voltaic cell</p> <p>D. all of them</p>
29	In which of the following components, pn-junction is used	<p>A. light emitting diode</p> <p>B. photo diode</p> <p>C. photo voltaic cell</p>

C. photo voltaic cell  
D. all of these

30

The circuit which is used to smooth the output voltage of the full-wave rectification is known as

A. transformer  
B. rectifier  
C. filter  
D. none of these