

ECAT Pre General Science Online Test

Sr	Questions	Answers Choice
1	For two resistance wires joined in parallel, the resultant resistance is $6/5$ ohm. When one of the resistance wire breaks, the effective resistance becomes 2 ohm. The resistance of the broken wire is	A. $3/5$ ohm B. 2 ohm C. $6/5$ ohm D. 3 ohm
2	A uniform resistance wire of Length L and diameter d has a resistance R. Another wire of same material has length, 4L and diameter 2d, the resistance will be	A. 2 R B. R C. R/2 D. R/4
3	Calculate the amount of charge flowing in 2 minutes in a wire of resistance 10Ω when a potential difference of 20 V is applied between its ends	A. 120 C B. 240 C C. 20 C D. 4 C
4	10^6 electrons are moving through a wire per second, the current developed is	A. 1.6×10^{-19} B. 1 A C. 1.6×10^{-15} A D. 10^{-6} A
5	The resistance of 20 cm long wire is 10Ω . When the length is changed to 40 cm. The new resistance is	A. 10Ω B. 20Ω C. 30Ω D. 40Ω
6	If two bulbs one of 60 W and other of 100 W are connected in parallel, then which one of the following will flow more?	A. 60 W bulb B. 100 W bulb C. Both equally D. None of these
7	Which one of the following causes production of heat when current is set up in a wire?	A. Fall of electrons from higher orbits to lower orbits B. Inter-atomic collisions C. Inter-electron collisions D. Collisions of conduction electron with atoms
8	Three resistors of resistance R each are combined in various ways. Which of the following cannot be obtained?	A. $3R$ B. $2R/4$ C. $R/3$ D. $2R/3$

		<div> <div></div> <div> <div></div> <div></div> </div> </div> <div> <div></div> <div></div> </div>
9	The resistance of the given conductor can be increased by	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>
10	A 100 W, 200 V bulb is connected to a 160 volts supply. The actual power consumption would be	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>
11	A 60 W bulb operates on 220 V supply. The current flowing through the bulb is	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>
12	At ordinary temperature, an increase in temperature increases the conductivity of	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>
13	Potentiometer is more sensitive than voltmeter, because	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>
14	A car battery has e.m.f 12 volt and internal resistance 5×10^{-2} ohm. If it draws 60 ampere current, the terminal voltage of the battery will be	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>
15	Specific resistance of a wire depends upon	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>
16	Cause of heat production in a current carrying conductor is	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>
17	In a building, there are 15 bulbs of 40 watts, 5 bulbs of 100 watts, 5 fans of 80 watts and a heater of 1 kilowatt. The voltage of the electric main is 220 volts. The minimum efficiency of the main fuse of the building will be	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>
18	The powers of tow electric bulbs are 100 W and 200 W. Both of them are joined with 220 V mains. The ratio of resistances of their filaments will be	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>
19	A 10 F capacitor is charged to a potential difference of 50 V and is connected to another uncharged capacitor in parallel. Now the common potential difference becomes 20 volt. The capacitance of second capacitor is	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>
20	A certain charge liberates 0.8 g of oxygen. The same charge will liberate. how many g of silver?	<div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div> <div> <div></div> <div></div> </div>

	silver :	C. 0.8 g D. 108/0.8 g
21	In a voltmeter the conduction takes place due to	A. Electrons only B. Holes only C. Electrons and holes D. Electrons and ions
22	A conducting wire is drawn to double its length. Final resistivity of the material will be	A. Double of the original one B. Half of the original one C. One fourth of the original one D. Same as original one
23	A piece of fuse wire melts when a current of 15 ampere flows through it. With this current. If it dissipates 22.5 W, the resistance of fuse wire will be	A. Zero B. $10\sqrt{3}\Omega$ C. $1\sqrt{3}\Omega$ D. $0.1\sqrt{3}\Omega$
24	If 2.2 kilowatt power is transmitted through a 10 ohm line at 22000 volt, the power loss in the form of heat will be	A. 0.1 watt B. 1 watt C. 10 watt D. 100 watt
25	The conductivity of a superconductor is	A. Infinite B. Very large C. Very small D. Zero
26	If 2.2 kilowatt power is transmitted through 1 10 ohm line at 22000 volt, the power loss in the form of heat will be	A. 0.1 watt B. 1 watt C. 10 watt D. 100 watt
27	A 50 volt battery is connected across 10 ohm resistor. The current is 4.5 A. The internal resistance of the battery is	A. Zero B. $0.5\sqrt{3}\Omega$ C. $1.1\sqrt{3}\Omega$ D. $5.0\sqrt{3}\Omega$
28	A (100 W , 200 W) bulb is connected to a 160 V power supply. The power consumption would be	A. 64 W B. 80 W C. 100 W D. 125 W
29	A wire of radius r has resistance R. If it is stretched to a wire of r/2 radius, then the resistance becomes	A. 2R B. 4R C. 16R D. Zero
30	Two electric bulbs of 200 W and 100 W have same voltage. If R_1 and R_2 be their resistance respectively then	A. $R_1 \leq 2R_2$ B. $R_2 \leq 2R_1$ C. $R_2 \leq R_1$ D. $R_1 \leq 4R_2$