

General Science 10th Class English Medium Chapter 8 Online Test

Sr	Questions	Answers Choice
1	Multi-meter is also called.	A. EVO B. OVE C. AVO D. VOA
2	Voltmeter is connected in.	A. Parallel position B. Series position C. Both a and b D. None of these
3	Voltmeter is used to.	A. Measure current B. Measure potential difference C. Measure voltage D. Both a and b
4	Ammeter is always connected with a circuit in.	A. parallal B. Series C. Both a and b D. None of these
5	Ammeter is used to.	A. Measure the current B. Detect the current C. Measrue the voltage D. None of them
6	Galvanometer is used to.	A. Detects the current B. Measure the current C. Measure the resistance D. Measrue the voltage
7	V_{S} / V_{D} is equal to.	A. Vp / Vs B. Np / Ns C. Ns / Np D. None
8	The SI uinit of Capacitance.	A. Farad B. Micro Farad C. Ohm D. Volt
9	Resistance ' R" is equal to.	A. I B. V C. V/I D. I/V
10	In Ohm's law V =	A. V/I B. I C. RI D. R/I
11	1 m A is equal to.	A. 10 ⁻³ A B. 10 ⁻⁶ A C. 10 ⁻² A D. 10 ⁻⁸ A
12	The unit of current in System International is.	A. Ampere B. Volt C. Ohm D. Newton
13	The device used for turning a circuit ON or OFF is.	A. Switch B. Fuse C. Circuit breaker D. Earth wire
14	The constant in Ohm's law is.	A. Current B. Resistance C. Potential difference D. Charge
15	The SI unit of resistence.	A. Ampere B. Volt C. Hertz D. Ohm