

Physics FSC Part 2 Chapter 13 Online MCQ's Test

Sr	Questions	Answers Choice
1	Drift velocity of electrons is.	A. 10^{-1} m/s B. 10^{-2} m/s C. 10^{-3} m/s D. 10^{-3} m/s
2	If 1×10^7 electrons passes through a conductor in 1.0 micro second , then the current is.	A. 2 A B. 1.6 A C. 2.6×10^{-6} A D. 1.6×10^{-6} A
3	A battery move a charge of 40 C around a circuit at constant rate in 20 Sec. The current will be.	A. 2 A B. 0.5 A C. 80 A D. 800 A
4	The potential difference between the head and tail of an electrical to	A. 600 Volt B. 700 Volt C. 800 Volt D. 900 Volt
5	Ampere second stands for the unit of.	A. Charge B. emf C. energy D. Power
6	A charged conductor has charge on its.	A. Inner surface B. Outer surface C. Middle surface D. Surrounding space
7	Thermosouple is an arrangement of two different metals:	A. Two convert heat energy into electrical energy B. To produce more heat C. To convert heat energy into chemical energy D. To convert electrical energy into heat energy
8	The powers of two electric bulbs are 100w and 200w. Which are connected to power supply of 220 V. The ratio of resistance of their filament will be:	A. 1:2 B. 2:3 C. 1:3 D. 4:3
9	The resistivity of two wires is ρ_1 and ρ_2 which are connected in series. If there dimentions are same then the equivalent resistivity of the combination will be:	A. $(\rho_1 + \rho_2)^2$ B. $1/\rho_1 + 1/\rho_2$ C. $\rho_1 + \rho_2$ D. $\rho_1 + \rho_2$

rgo(34, 34, 34); >p^{1/}p₂

-
- 10 A wire uniform cross-section. A length L and resistance R is cut into two equal parts. The resistivity of each part will be:
- A. Doubled
B. Halved
C. Remain the same
D. One fourth
-
- 11 When a wire is stretched and its radius becomes $r/2$, then its resistance will be
- A. 16 R
B. 4 R
C. 2R
D. 0
-
- 12 10⁶ electrons are moving through a wire per second the current developed is:
- A. 1.6×10^{-19} A
B. 1 A
C. 1.6×10^{-13} A
D. 10⁶ A
-
- 13 Calculate current in $2R / 4\Omega$ resistor.
- A. 1 A
B. $2R / 4\Omega$
C. $R/3\Omega$
D. $2R / 3\Omega$
-
- 14 Three resistors of resistance R each are combined in various ways, Which of the following cannot be obtained?
- A. $3 R\Omega$
B. $2R / 4\Omega$
C. $R/3\Omega$
D. $2R / 3\Omega$
-
- 15 Seven resistances are connected as shown in the figures . THe equivalent resistance between A and B is:
- A. 3Ω
B. 4Ω
C. 4.5Ω
D. 5Ω
-
- 16 The unit of resistance is:
- A. Ω
B. Ωm
C. $\Omega^{⁻¹}m^{⁻¹}$
D. $\Omega m^{⁻¹}$
-
- 17 Semiconductor diodes are called:
- A. Ohmic
B. non ohmic
C. Both a & b
D. none of above