

Physics FSC Part 2 Chapter 16 Online MCQ's Test

Sr .	Questions	Answers Choice
1	The peak to peak value of alternating voltage is	A. 2V _o B. V _o D. None of these
2	The value of capacitive reactance is given by	A. Xc = VI B. xc= 1/wc or xc= wL C. xc= 1*wc or xc=Lw D. All of above
3	If $I_{\rm O}$ is the peak value of current, then its root mean square value is given by	B. 2 l _o C. l _o D. 0.7 l _o
4	If V_{rms} be the root mean square value of emf then its peak to peak value is given by	