

Physics 10th Class English Medium Online Test

Sr	Questions	Answers Choice
1	If we double both the current and the voltage in a circuit while keeping its resistance constant, the power:	A. class="MsoNormal">Remains unchanged</p></p> B. class="MsoNormal">Halves</p></p> C. class="MsoNormal">Doubles</p></p> D. class="MsoNormal">Four time</p></p>
2	When we double the voltage in a simple electric circuit, we double the:	A. class="MsoNormal">Current</p></p> B. class="MsoNormal">Power</p></p> C. class="MsoNormal">Resistance</p></p> D. class="MsoNormal">Both a and b</p></p>
3	Electric potential and e.m.f.:	A. class="MsoNormal">Are the same terms</p></p> B. class="MsoNormal">Are the different terms</p></p> C. class="MsoNormal">Have different units</p></p> D. class="MsoNormal">Both b and c</p></p>
4	Why household appliances should be connected in parallel with the voltage source:	A. class="MsoNormal">To increase the resistance of the circuit</p></p> B. class="MsoNormal">To decrease the resistance of the circuit</p></p> C. class="MsoNormal">To provide each appliance the same voltage as the power source</p></p> D. class="MsoNormal">To provide each appliance the same current as the power source</p></p>
5	What happens to the intensity or the brightness of the lamps connected in series as more and more lamps are added:	A. class="MsoNormal">Increases</p></p> B. class="MsoNormal">Decreases</p></p> C. class="MsoNormal">Remains the same</p></p> D. class="MsoNormal">Cannot be predicted</p></p>
6	What is the voltage across a 6 Ω resistor when 3 A of current passes through it:	A. class="MsoNormal">2 V</p></p> B. 9V C. 18 V D. 36 V
7	If a dielectric medium is present between two point charges then electrostatic force will be:	A. class="MsoNormal">Increased</p></p> B. class="MsoNormal">Decreased</p></p> C. class="MsoNormal">Vanishes</p></p> D. class="MsoNormal">Remain same</p></p>
8	The substances which do not have free electrons are called:	A. class="MsoNormal">Insulators</p></p> B. class="MsoNormal">Conductors</p></p> C. class="MsoNormal">Semiconductors</p></p> D. class="MsoNormal">None of

9	The electric potential energy per unit charge is called:	A. <p class="MsoNormal">Electric field<o:p></o:p></p> B. <p class="MsoNormal">Electric potential<o:p></o:p></p> C. <p class="MsoNormal">Electric intensity<o:p></o:p></p> D. <p class="MsoNormal">All of above<o:p></o:p></p>
10	A unit of electric charge, equal to the charge of 6.25×10^{18} electrons is:	A. <p class="MsoNormal">Electricity<o:p></o:p></p> B. <p class="MsoNormal">Coulomb<o:p></o:p></p> C. <p class="MsoNormal">Electric potential<o:p></o:p></p> D. <p class="MsoNormal">Volt<o:p></o:p></p>
11	Capacitors are mainly used for radio frequency tuning:	A. <p class="MsoNormal">Paper capacitor<o:p></o:p></p> B. <p class="MsoNormal">Air capacitor<o:p></o:p></p> C. <p class="MsoNormal">Mica capacitor<o:p></o:p></p> D. <p class="MsoNormal">Electrolytic capacitor<o:p></o:p></p>
12	A paper capacitor is usually available in the form of:	A. <p class="MsoNormal">Tubes<o:p></o:p></p> B. <p class="MsoNormal">Rolled foil<o:p></o:p></p> C. <p class="MsoNormal">Disc<o:p></o:p></p> D. <p class="MsoNormal">Plates<o:p></o:p></p>