

Physics FSC Part 2 Online MCQ's Test

Sr	Questions	Answers Choice
1	In metal detector, we use.	A. L-C circuit B. R-L circuit C. R-C circuit D. RLC series circuit
2	In three phase voltage across any two lines is about.	A. 220 V B. 230 V C. 400 V D. 430 V
3	In three phase A.C supply coils are inclined at an angle of.	A. 0° B. 90° C. 120° D. 80°
4	In three phase A.C. generator the phase difference between each pair of coil is.	A. 45° B. 90° C. 120° D. 60°
5	In RLC circuit the energy is dissipated in	A. R only B. R and L C. R and C D. L and C
6	A resistance frequency the impedance of RLC parallel circuit is.	A. Zero B. Infinite C. Maximum D. Minimum
7	The circuit which compares the two voltages is.	A. LDR B. Sensor C. Comparator D. Logic gate
8	In RLC series circuit at resonance the phase difference between capacitor and inductor reactance is.	A. 90° B. 270° C. 0° D. 180°
9	The power factor of RL series circuit is.	A. 0 B. 1 C. Less than 1 D. More than one
10	At resonance frequency, the impedance of RLC series circuit is.	A. Maximum B. Minimum C. Zero D. Infinite
11	X_L is low for low frequency f but X_C is.	A. Zero B. Low C. High D. Same is H
12	Which consumes small power.	A. Inductor B. Resistor C. Motor D. All of these
13	The expression $P = VI$ hold only when current and voltage are.	A. In phase B. Out of phase C. At right angle to each other D. At angle of 120°
14	Power dissipated in a pure inductor is.	A. Large B. Small C. Infinite D. Zero
15	At resonance, the behavior of R-L-C series circuit is.	A. Resistive B. Capacitive C. Inductive D. Modulative

16	The phase angle of a series RLC circuit at resonant frequency is	A. $1/2$ B. σ C. Zero D. $\sigma/4$
17	The unit of impedance is.	A. Henry B. Hertz C. Ampere D. Ohm