

## CS-302 Quiz Preparation Virtual University

Sr	Questions	Answers Choice
1	Given the state diagram of an up/down counter, we can find _____	<p>A. The next state of a given present state</p> <p>B. The previous state of a given present state</p> <p>C. Both the next and previous states of a given state</p> <p>D. The state diagram shows only the inputs/outputs of a given states</p>
2	_____ is said to occur when multiple internal variables change due to change in one input variable	<p>A. Clock Skew</p> <p>B. Race condition</p> <p>C. Hold delay</p> <p>D. Hold and Wait</p>
3	74HC163 has two enable input pins which are _____ and _____	<p>A. ENP, ENT</p> <p>B. ENI, ENC</p> <p>C. ENP, ENC</p> <p>D. ENT, ENI</p>
4	Flip flops are also called _____	<p>A. Bi-stable dualvibrators</p> <p>B. Bi-stable transformer</p> <p>C. Bi-stable multivibrators</p> <p>D. Bi-stable singlevibrators</p>
5	The divide-by-60 counter in digital clock is implemented by using two cascading counters	<p>A. Mod-6, Mod-10</p> <p>B. Mod-50, Mod-10</p> <p>C. Mod-10, Mod-50</p> <p>D. Mod-50, Mod-6</p>
6	In a sequential circuit the next state is determined by _____ and _____	<p>A. State variable, current state</p> <p>B. Current state, flip-flop output</p> <p>C. Current state and external input</p> <p>D. Input and clock signal applied</p>
7	A frequency counter _____	<p>A. Counts pulse width</p> <p>B. Counts no. of clock pulses in 1 second</p> <p>C. Counts high and low range of given clock pulse</p> <p>D. None of given options</p>
8	A positive edge-triggered flip-flop changes its state when _____.	<p>A. Low-to-high transition of clock</p> <p>B. High-to-low transition of clock</p> <p>C. Enable input (EN) is set</p> <p>D. Preset input (PRE) is set</p>
9	In order to synchronize two devices that consume and produce data at different rates, we can use _____	<p>A. Read Only Memory</p> <p>B. First In First Out Memory</p> <p>C. Flash Memory</p> <p>D. Fast Page Access Mode Memory</p>
10	in _____, all the columns in the same row are either read or written.	<p>A. Sequential Access</p> <p>B. MOS Access</p> <p>C. FAST Mode Page Access</p> <p>D. None of given options</p>